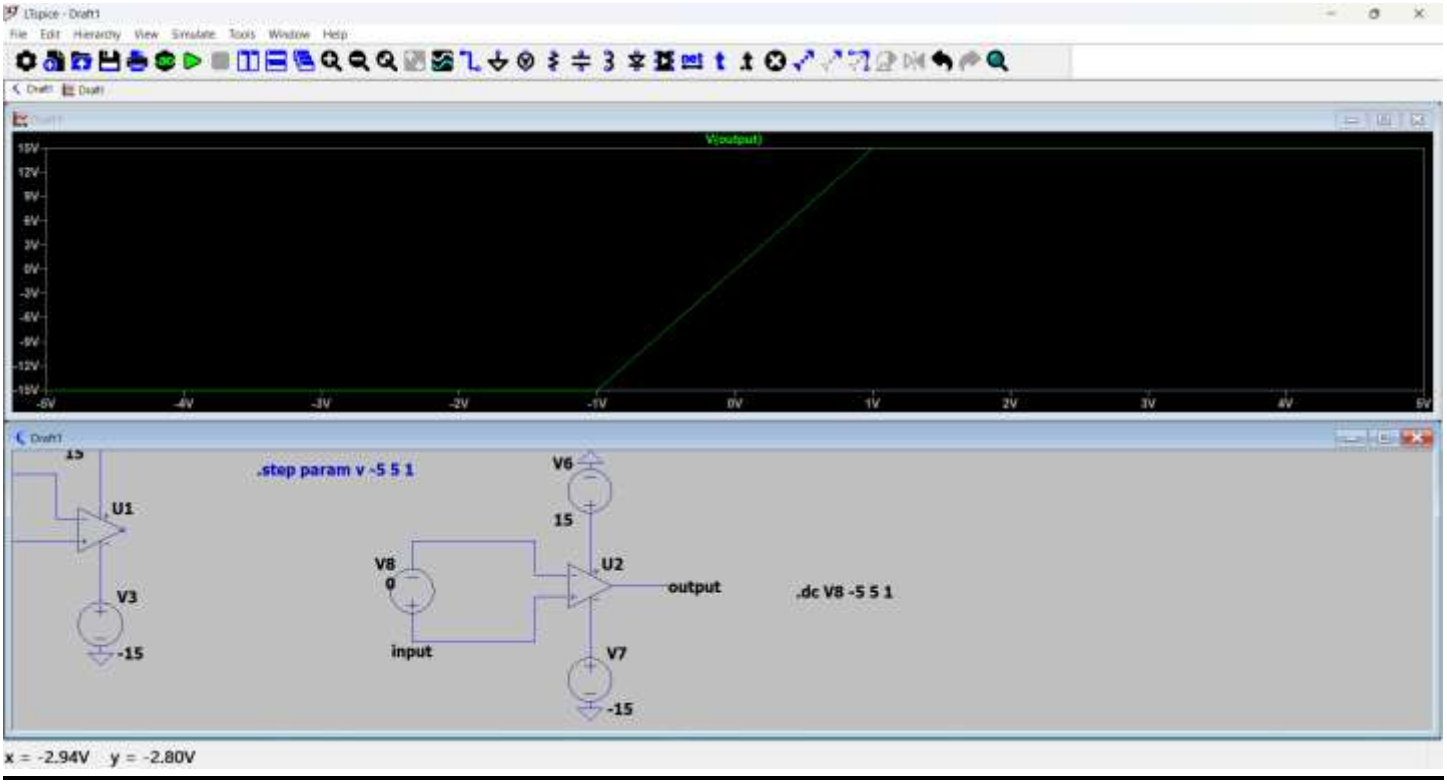
Ain Shams University
Faculty of Engineering
Electronics & Comm. Eng. Dept.




Experiment (2) Report

Names	IDs	Department	Attendance slot	Group No.	Group Code Part
Abdelrahman sherif	2300100	ECE	even	29	D6
Amr hatem	2300729	ECE			
Abdelrahman Mohamed ali	2300518	ECE			

Draw the comparator Transfer function. (1 Mark)




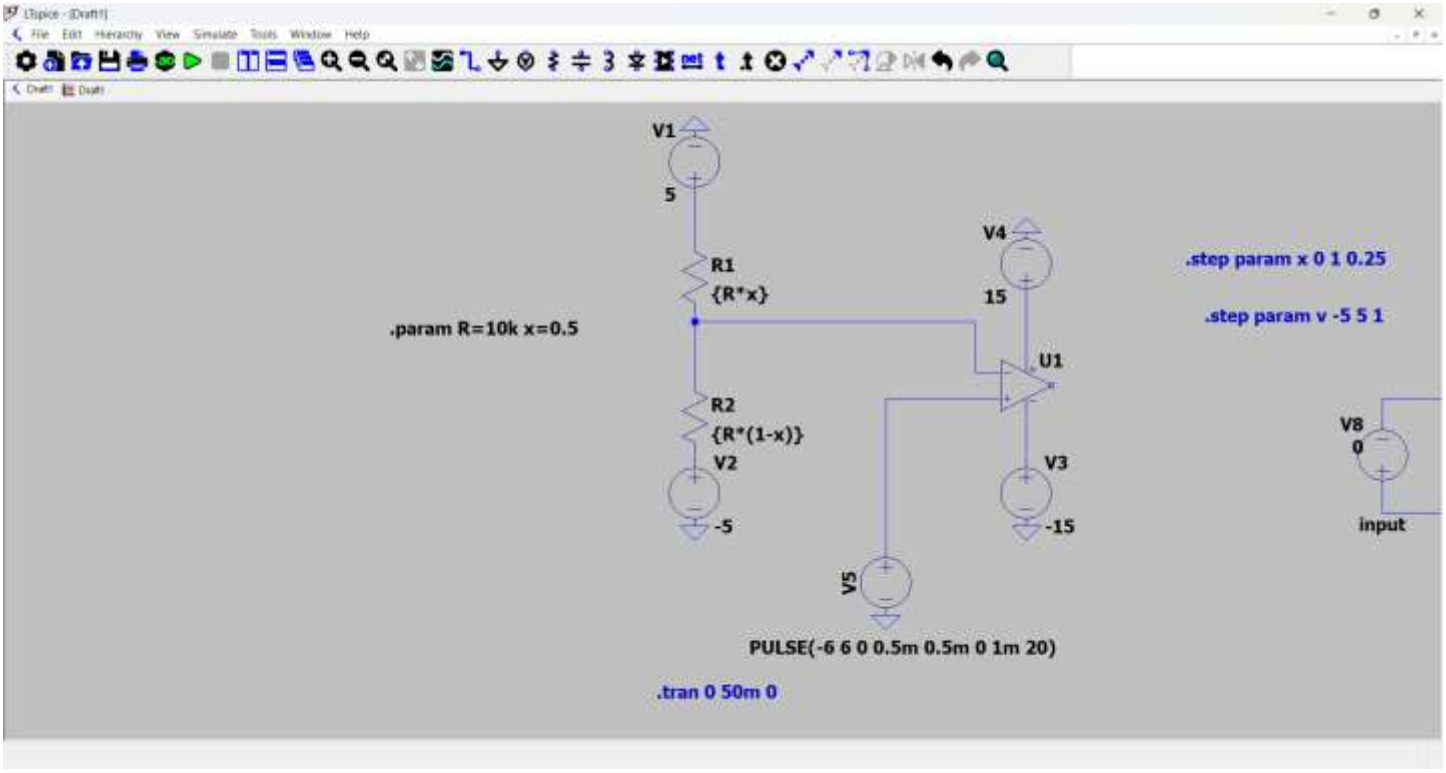2. Snapshot the schematic of the comparator circuit of Figure 21.




3. Snapshot for Reference voltage (output of potentiometer), Input and Output for 5 different positions of reference voltage 5, 2.5, 0, –2.5, –5 V. (2 Marks).

a)position 1

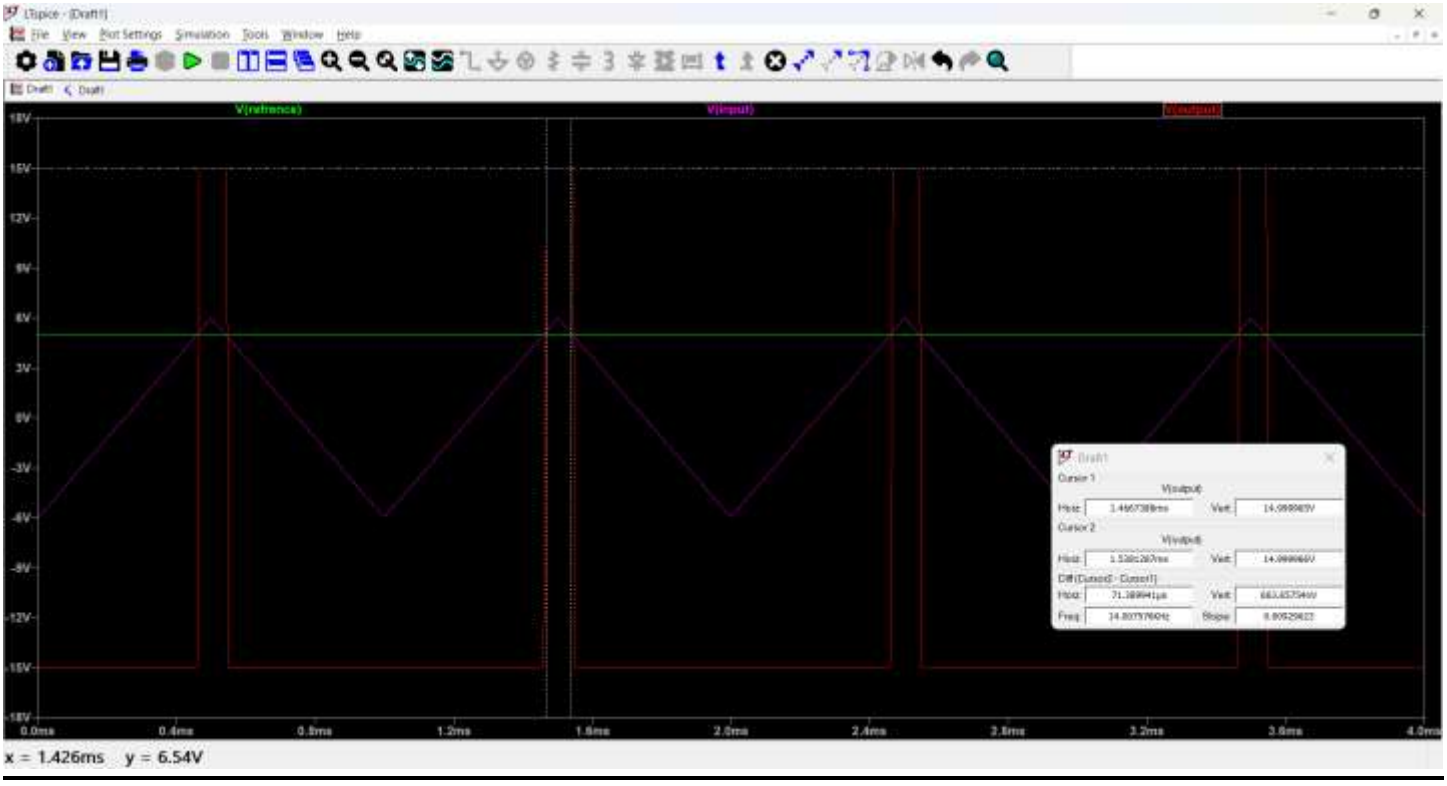


Duty cycle = 7.1%

b) position 2

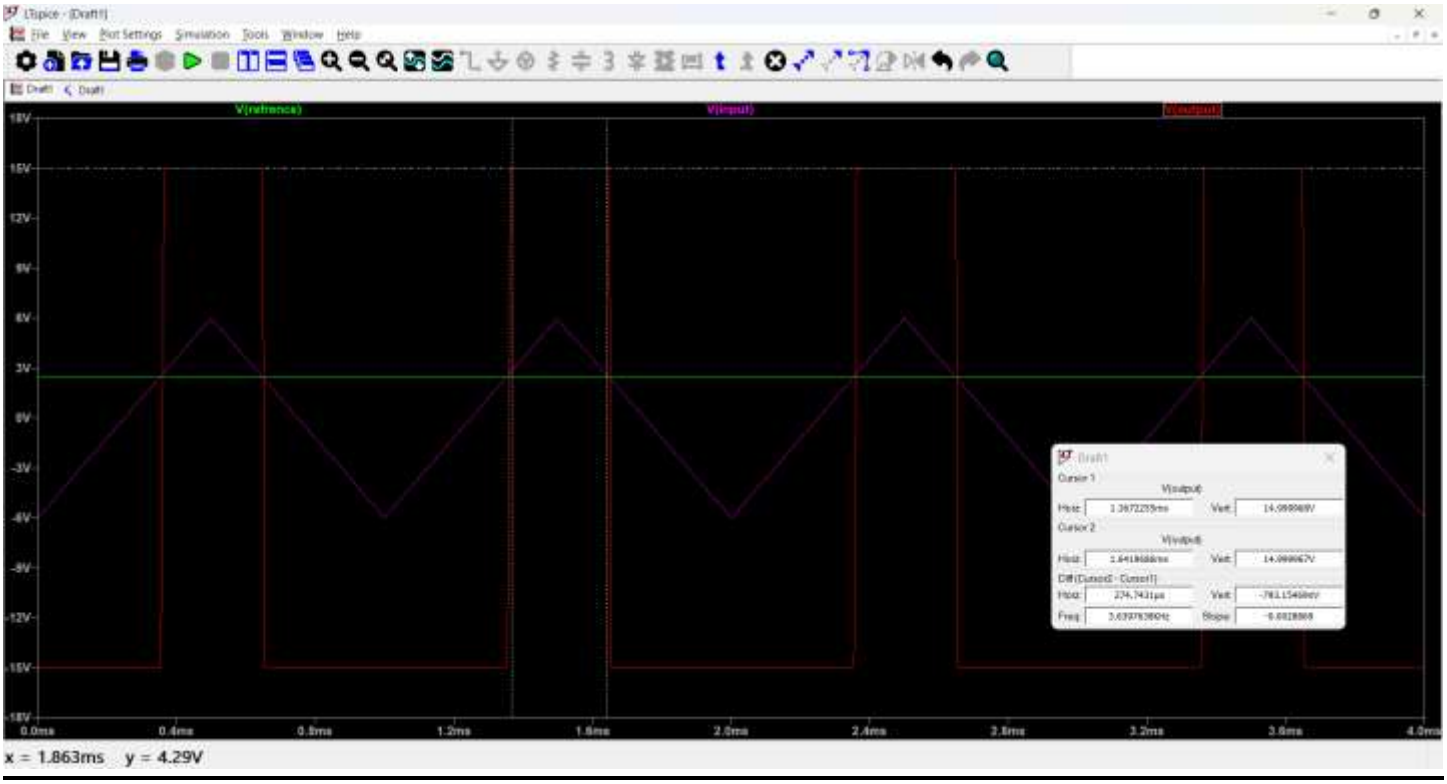


Duty cycle = 27.5%

c) position 3

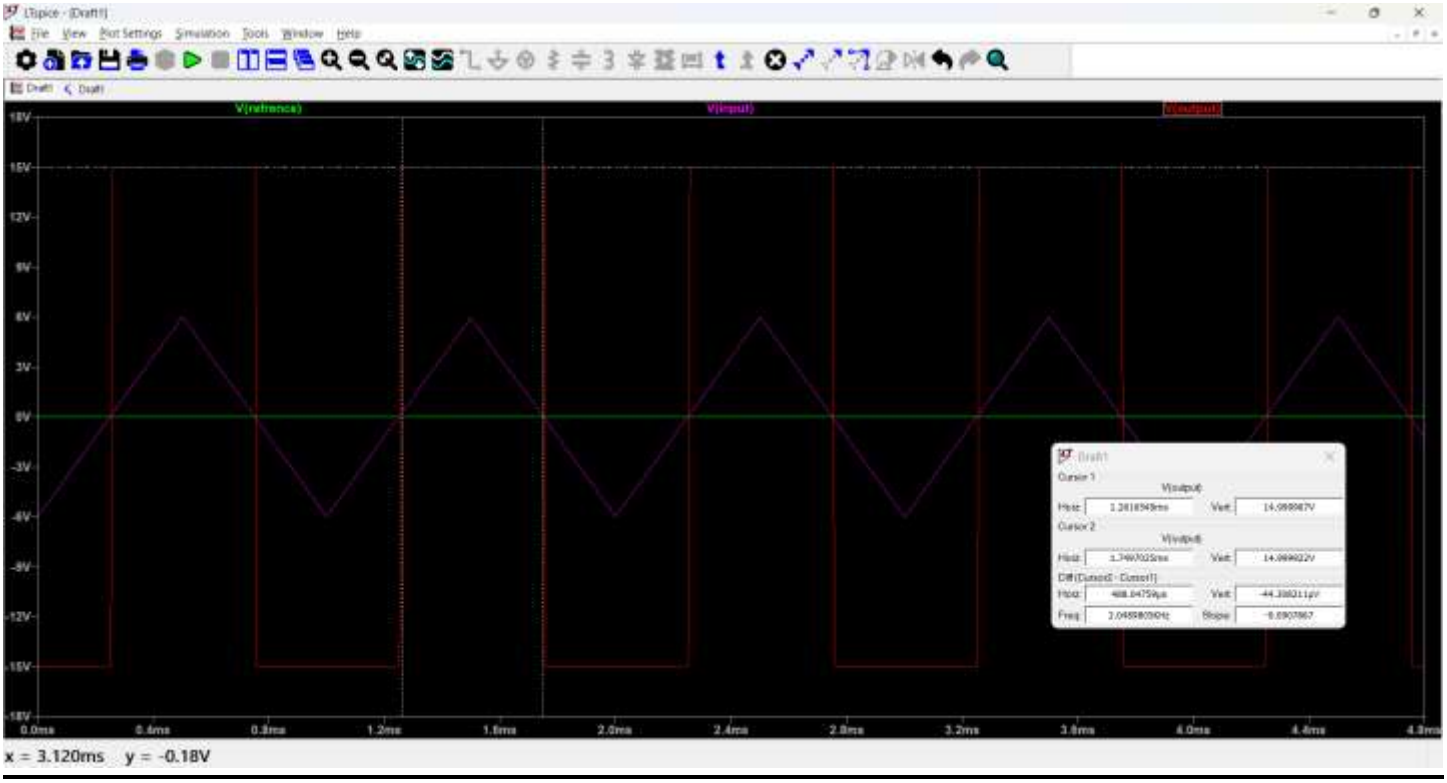


Duty cycle = 49%

d) position 4

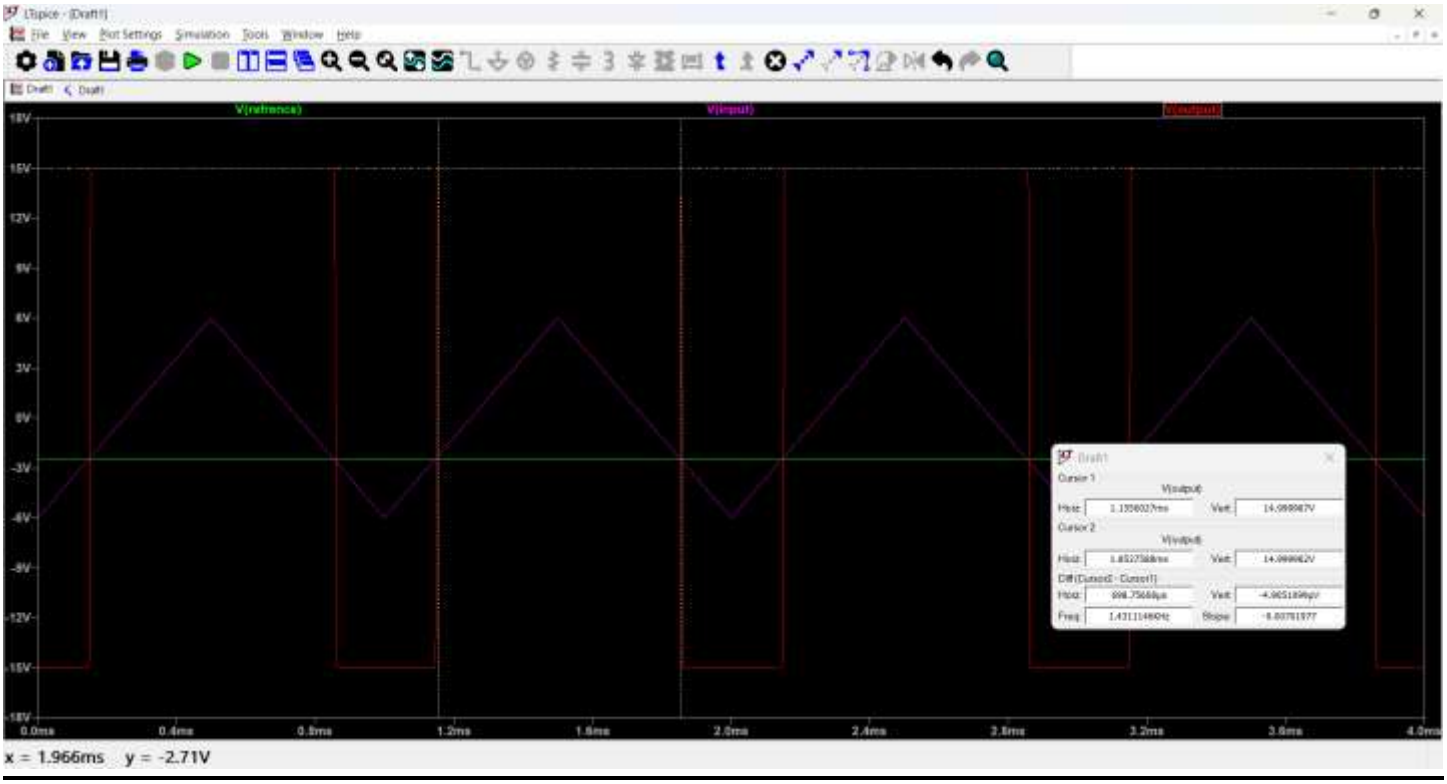

Duty cycle = 70%

e)position 5

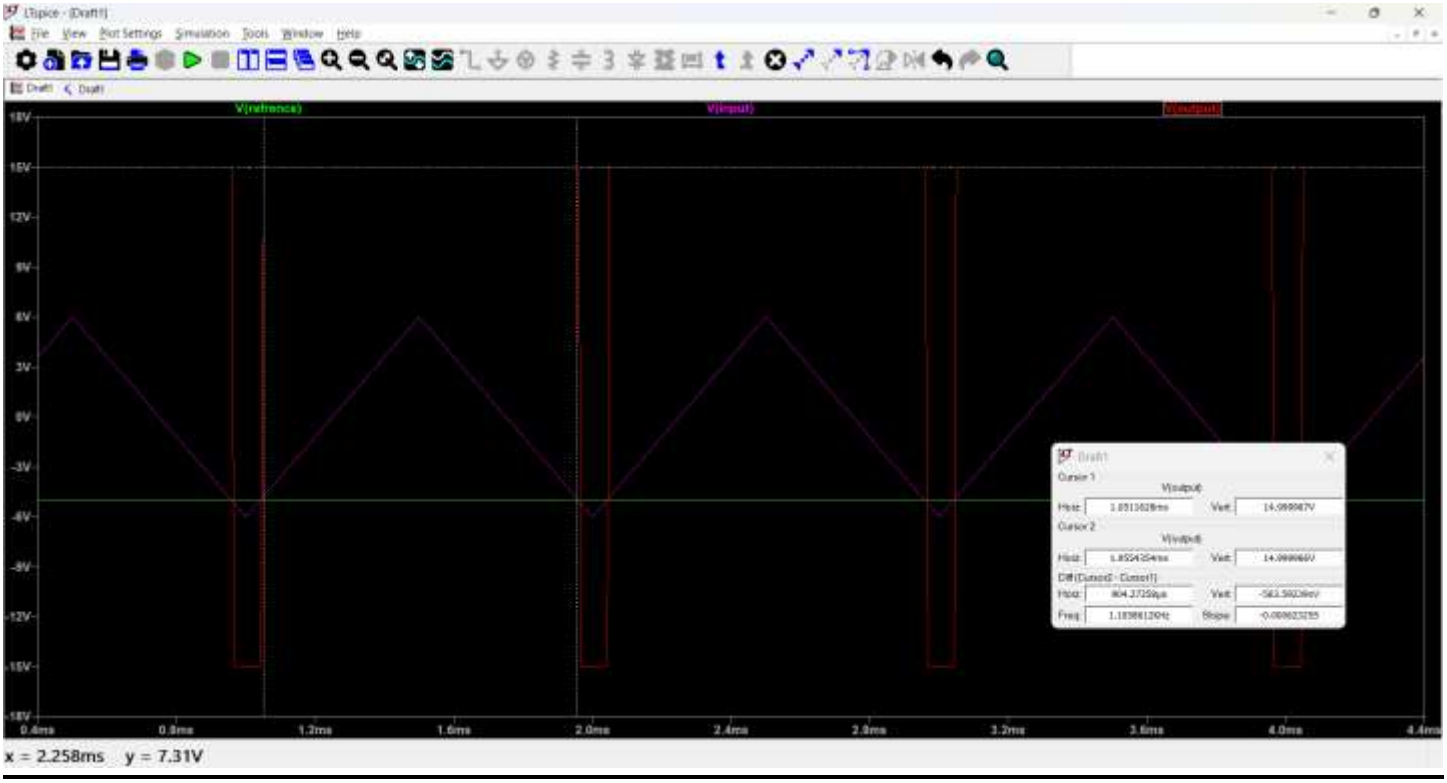

Duty cycle = 90.4%