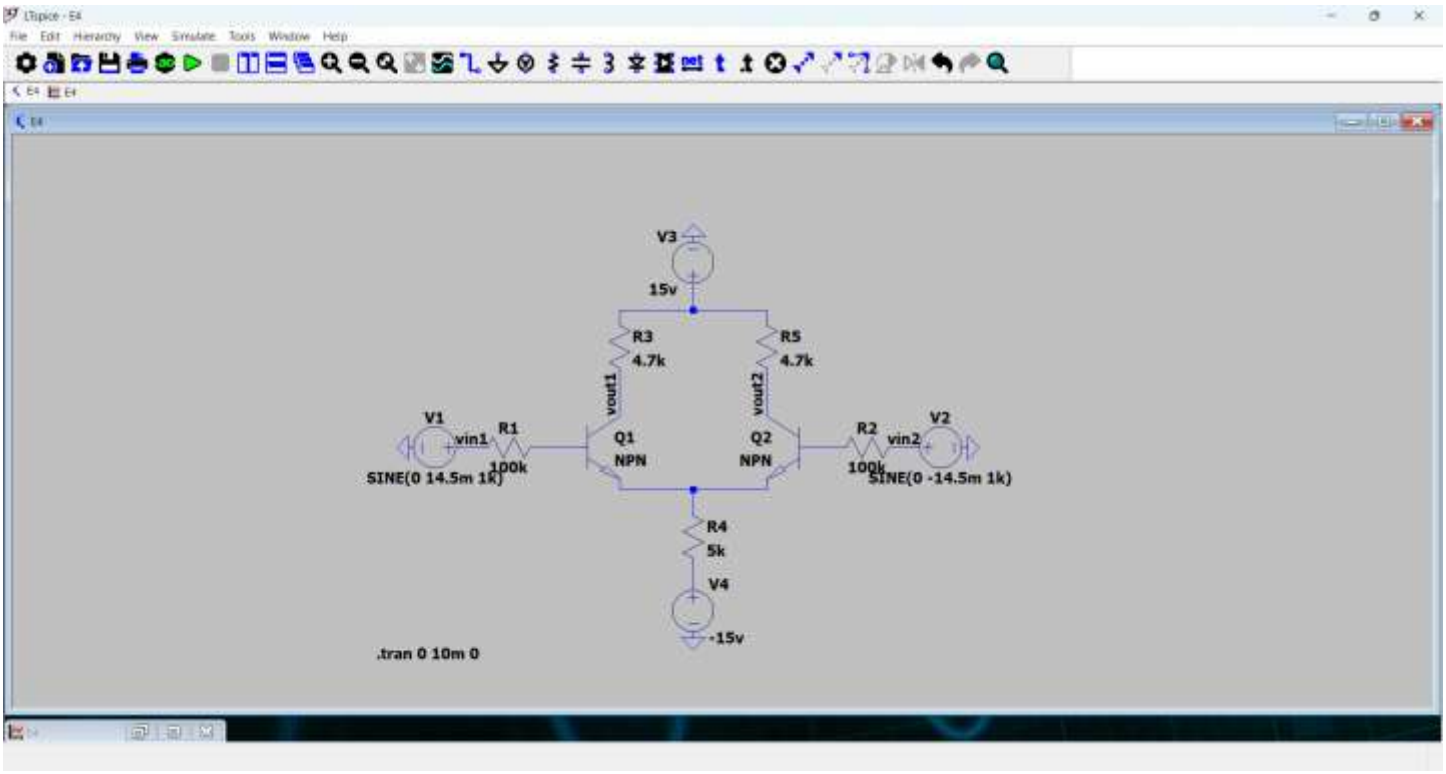
Ain Shams University
Faculty of Engineering
Electronics & Comm. Eng. Dept.



Experiment (4) Report

Names	IDs	Department	Attendance slot	Group No.	Group Code Part
Abdelrahman sherif	2300100	ECE	even	29	A29
Amr hatem	2300729	ECE			
Abdelrahman Mohamed ali	2300518	ECE			

1. The schematic of the circuit shown drawn in the simulator (1 Mark):




2. Snapshot displaying Vin1, Vin2 and Vout1 waveforms.(Vin1 = Vin2 is Sine wave with 1KHz frequency and x mV-PP). (1 Mark):

DC values:



AC values

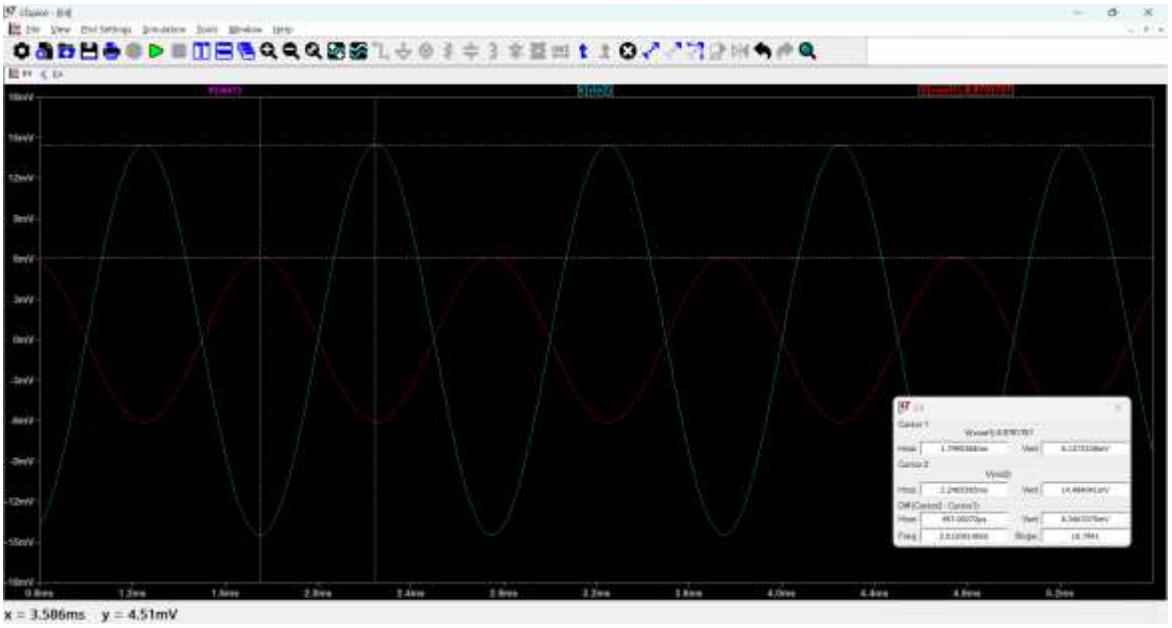


3. Snapshot displaying V1, V2 and Vout waveforms. (V1 = -V2 is Sine wave with 1KHz frequency and x mV-PP). (1 Mark):

DC values



AC values

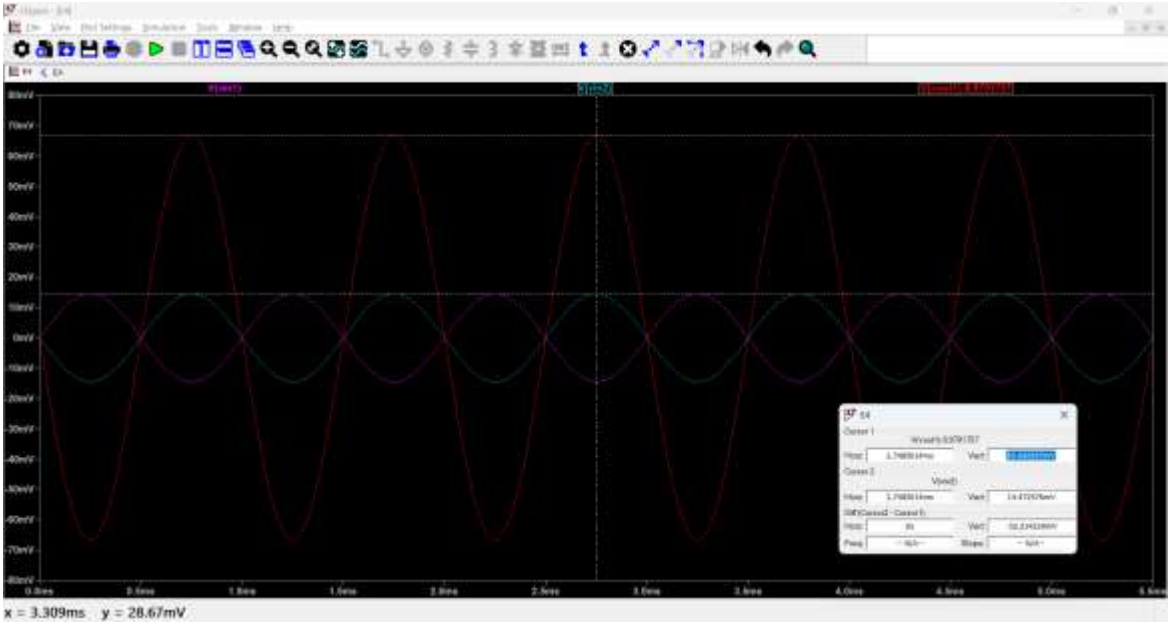

4. Calculate the CMRR. (1 Mark):

Av DM = 66.7/14.47 = 4.61

Av CM = 6.137/14.484 =0.424

CMRR= Av DM / Av CM = 4.61/0.424 = 10.87

5. Derive the differential and common mode gain. (1 Mark):

