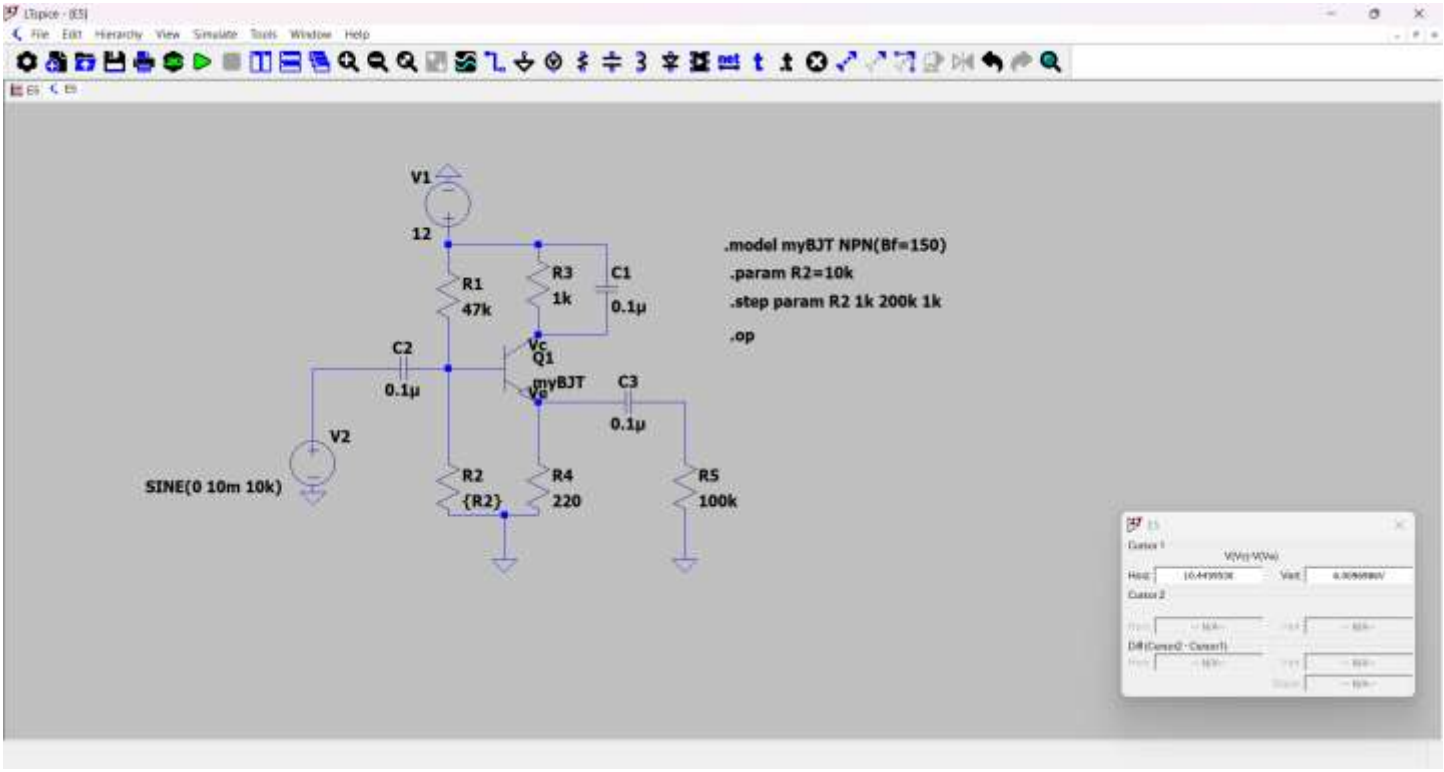
Ain Shams University
Faculty of Engineering
Electronics & Comm. Eng. Dept.



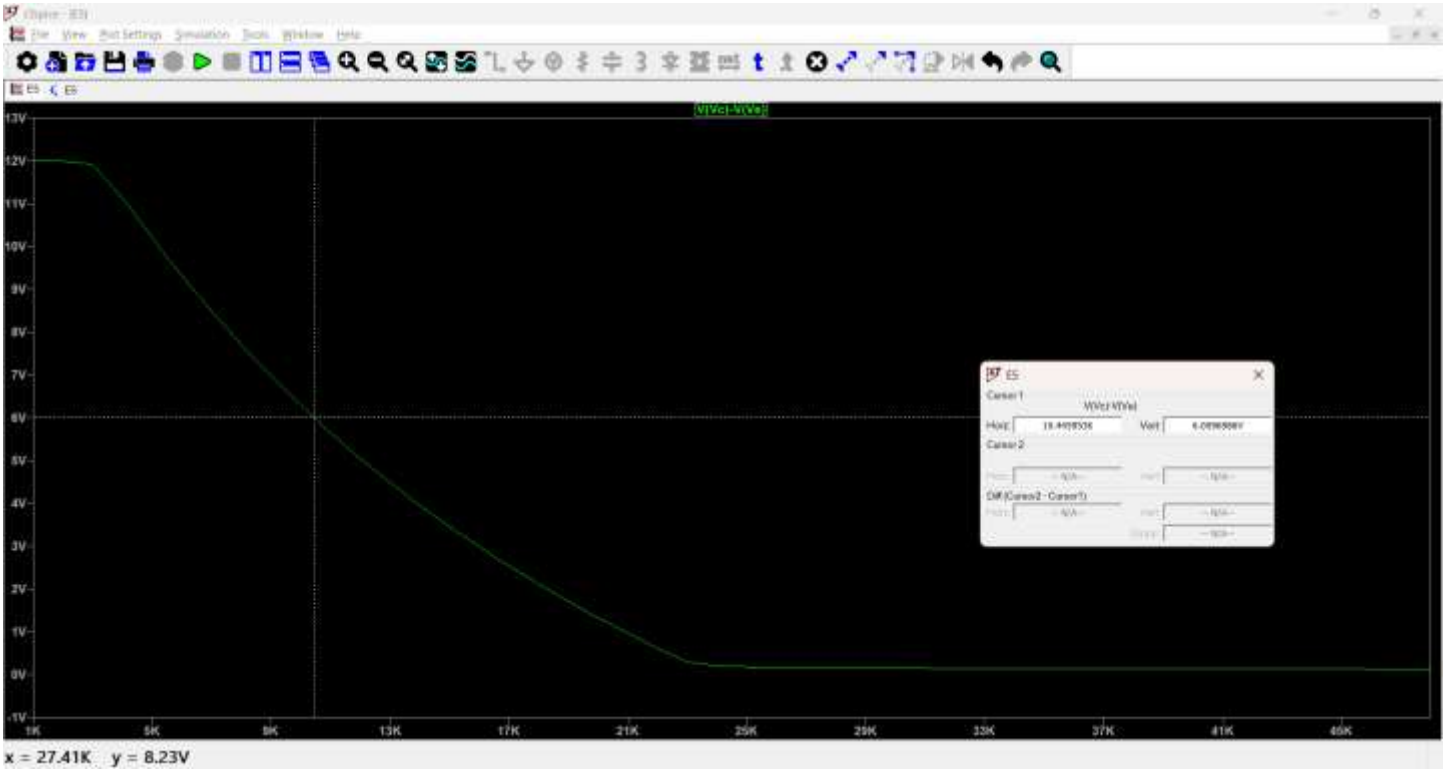

# Experiment (5) Report

| Names | IDs | Department | Attendance slot | Group No. | Group Code Part |
|---|---|---|---|---|---|
| Abdelrahman sherif | 2300100 | ECE | even | 29 | B10 |
| Amr hatem | 2300729 | ECE | | | |
| Abdelrahman Mohamed ali | 2300518 | ECE | | | |

# 1. The schematic of the circuit shown drawn in the simulator (1 Mark):




## 2. Tune the circuit till VCE ~ VCC/2. Report the DC value of VCE through a snapshot (1 Mark).




R2=10.453558K
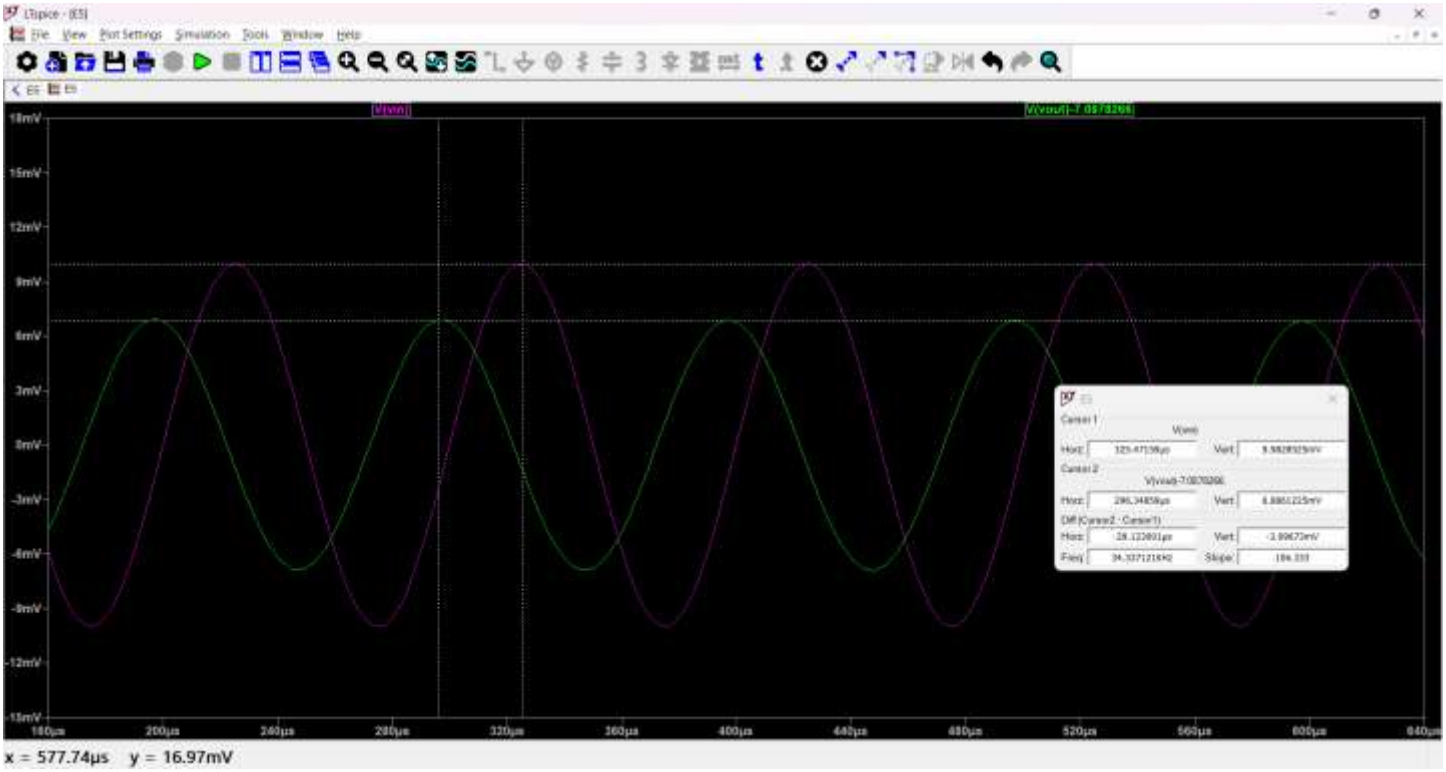
## 3. Snapshot shows the input and the output waveforms (1Mark).




## 4. Measure the gain from simulation results in (3) (1 Mark).

Av=0.689795

**5. By Hand-analysis, calculate Ib and Ic. Derive the gain formula and calculate it. Compare analytical and simulation results (1 Mark).**

